



Printed Pages : 7

TEC-201/101

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3034

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. II) EXAMINATION, 2007-08

ELECTRONIC ENGINEERING

Time : 3 Hours]

[Total Marks : 100

- Note :**
- (1) Attempt **all** questions.
 - (2) All question carry **equal** marks.
 - (3) In case of numerical problems assume data whenever not provided.
 - (4) Be precise in your answer.

1 Attempt any **four** parts :

5×4

- (a) The mobility of free electrons and holes in pure germanium are 3800 and 1800 m^2 / Vs respectively. The corresponding values for pure silicon are 1300 and 500 m^2 / Vs respectively. Determine the values of intrinsic conductivity for both. Assume $n_i = 2.5 \times 10^{13} \text{ cm}^{-3}$ for germanium and $n_i = 2.5 \times 10^{10} \text{ cm}^{-3}$ for silicon at room temperature.
- (b) Describe the difference between majority and minority carriers.
- (c) Define the static and dynamic resistance of the diode, how these resistances are measured.



- (d) Discuss the difference between diffusion and transition capacitances.
- (e) Draw the reverse characteristics of a diode; define avalanche and Zener breakdown regions.
- (f) Define the reverse recovery time of a diode.

2 Attempt any **four** parts of the following :

5×4

- (a) Sketch V_o for the circuit shown in **fig. 1** D1 and D2 are silicon diodes.

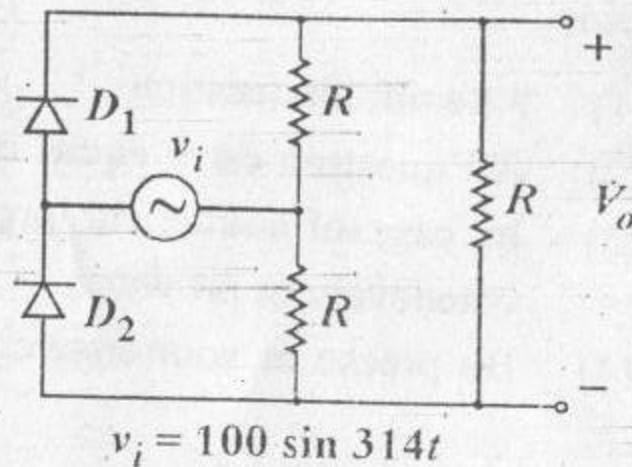


Fig. 1

- (b) For the circuit shown in **fig. 2** sketch i_R and V_o . (D1 and D2 are Si diode.)

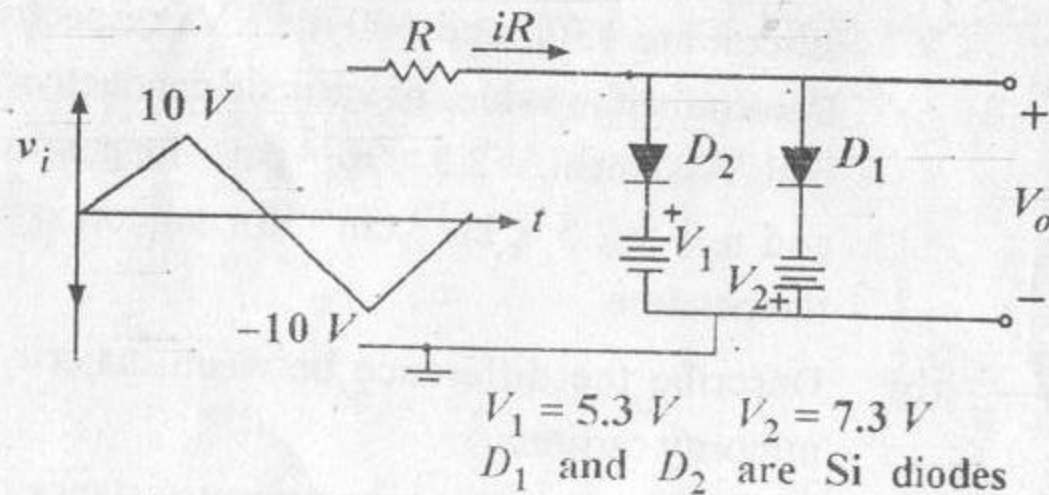


Fig. 2

- (c) Determine V_L , I_L , I_Z and I_R for the circuit R_L is 470 ohms.

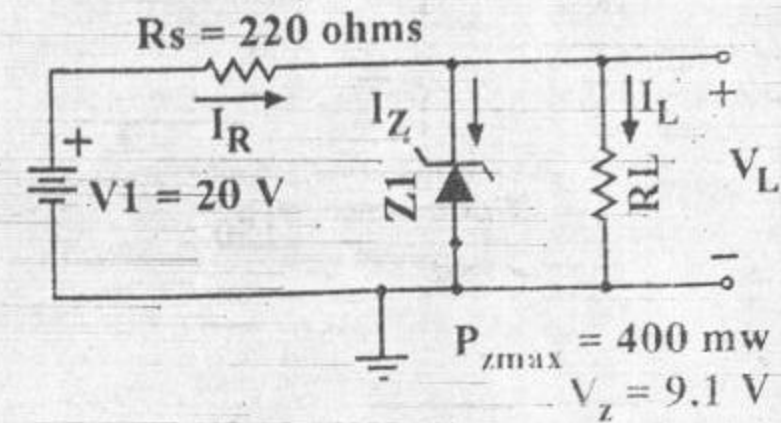


Fig. 3

- (d) For the clamping circuit shown in **fig. 4** sketch for V_o .

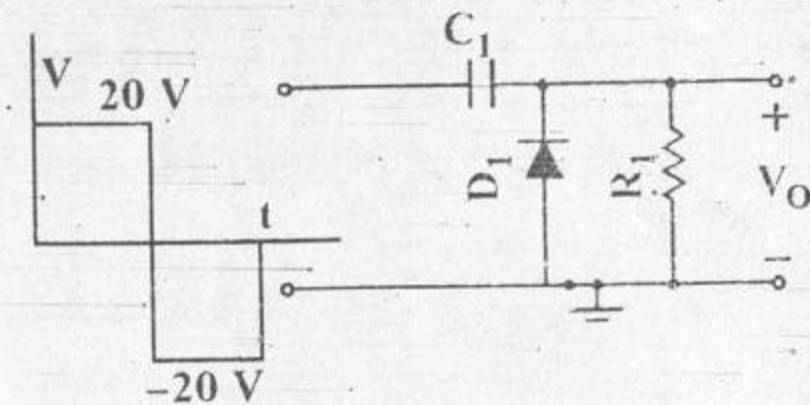


Fig. 4

- (e) Draw the circuit diagram of a bridge rectifier. Discuss the operation and find dc and rms output voltage.
- (f) With the help of the circuit diagram explain the working of a voltage doubler.

3 Attempt any **two** parts of the following :

10×2

- (a) For a voltage divider biasing circuit shown in **fig. 5**. Find I_C , V_{CE} , I_B , V_E and V_B .



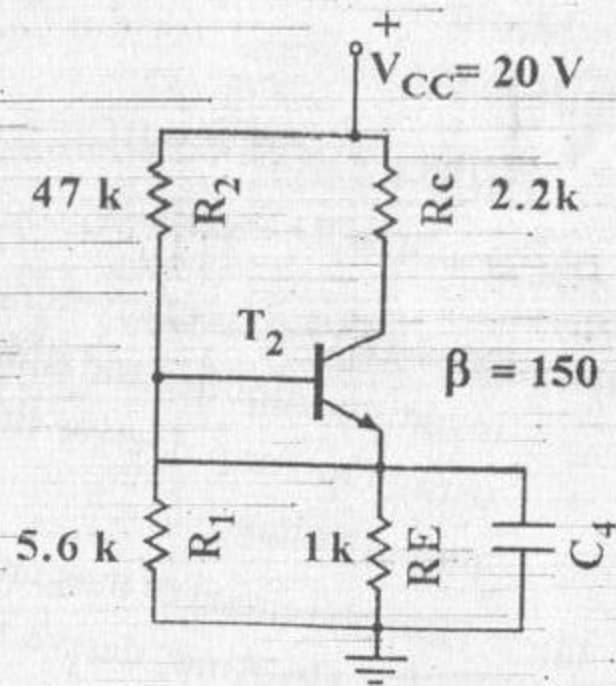


Fig. 5

- (b) For the circuit shown in fig. 6. Find A_v , A_i , Z_o and Z_i . (h) parameters are $h_{ie} = 1k$, $h_{re} = 0$, $h_{fe} = 50$, $h_{oe} = 0$.

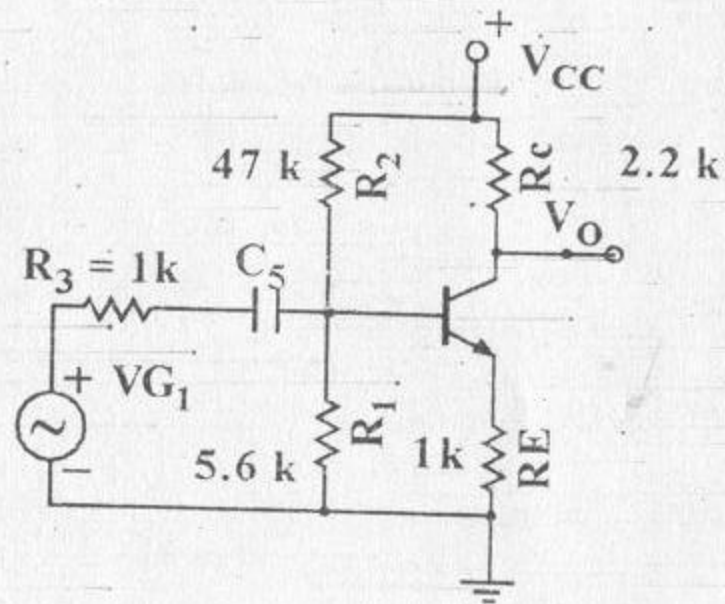


Fig. 6

- (c) Derive the expression for input impedance and voltage gain for a CE and shown in fig. 7 using simplified (approximate) equivalent circuit i.e. $h_{re} = h_{oe} = 0$.

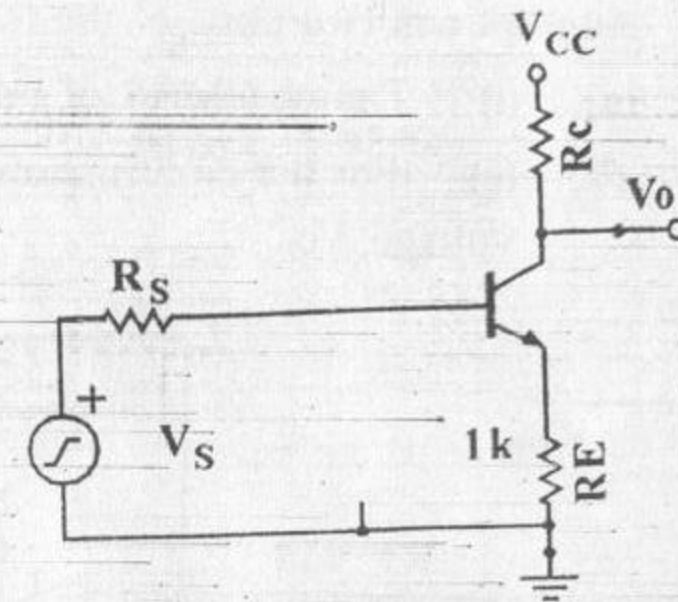


Fig. 7

- 4 Attempt any **two** parts of the following : 10×2
- (a) Define trans conductance (g_m) output resistance (r_p) and gain of a FET. How these parameters are determined graphically.
- (b) For common source FET amplifier with source resistance is R_s . Derive the expression for voltage gain input impedance and output impedance.
- (c) For a circuit shown in fig. 8. Calculate V_o , Z_i and Z_o . Input is $V_i = 0.2V$ (rms.)
 $I_{DSS} = 9mA$, $V_p = -4.5V$.

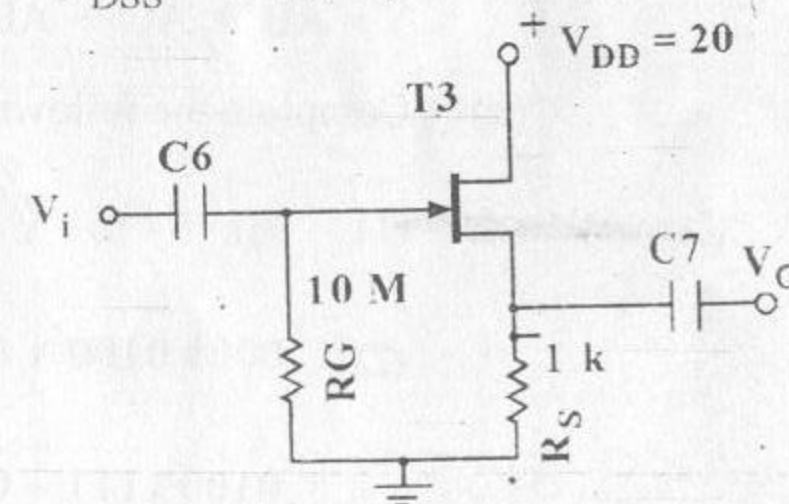


Fig. 8

5 Attempt any two parts of the following :

10×2

- (a) (i) Define CMRR of a differential amplifier.
 (ii) For the circuit shown in fig. 9. Find out voltage, V_o .

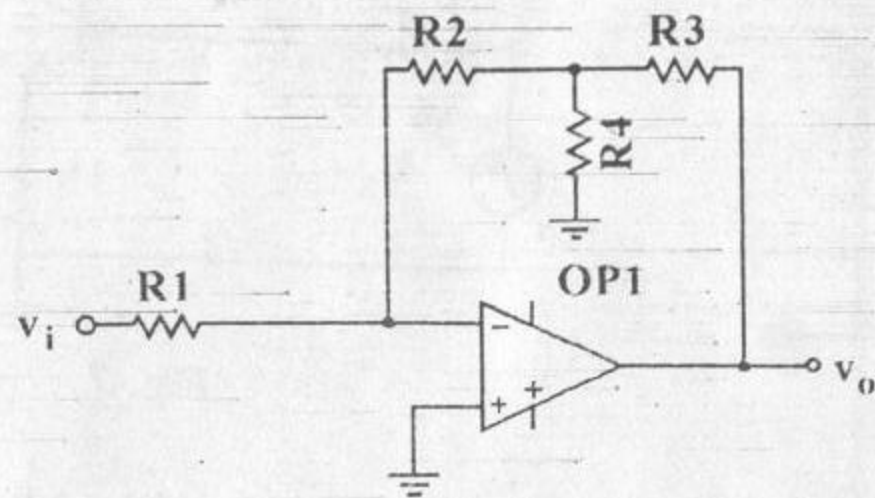


Fig. 9

- (b) (i) Convert the following numbers :

(1) $2D6_{16} = ()_2$

(2) $011010110_2 = ()_{16}$

- (ii) Convert the following function in to canonical forms :

$$Y = AB + AC + AD + BCD$$

- (iii) Complete the following operations :

(1) $8_{16} + F_{16} = ()_{16}$

(2) $0001\ 0100 + 0011\ 1001 = ()_2$

$0100\ 1111 - 0000101 = ()_2$

- (iv) Minimize the following function using Boolean algebra.

$$Y = \bar{A}BCD + AB\bar{C}\bar{D} + AB\bar{C}D + ABCD + ABC\bar{D} + A\bar{B}\bar{C}D + A\bar{B}CD + A\bar{B}C\bar{D}$$

- (c) (i) Draw the circuits of inverting amplifier, non-inverting amplifier and difference amplifier using Op-Amp. Derive the expression for output voltage.
 (ii) Draw the circuit of integrator and differentiator using Op-Amp, derive the expression for output.

